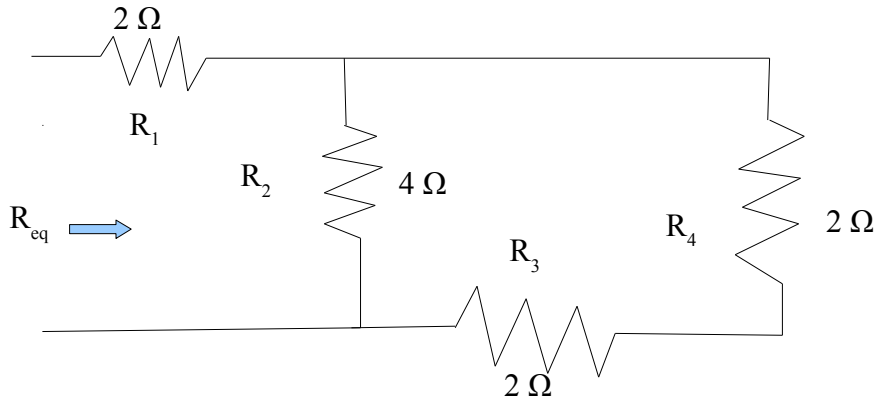


**Exam #1 Rework**  
by Zack Smith  
September 30<sup>th</sup>, 2012  
ECE 2312: Electrical Engineering Science I


## Problem #1a:

Compute the equivalent resistance for the network shown below:




Firstly, we know  $R_3$  and  $R_4$  are in series, giving us a new equivalent resistor:
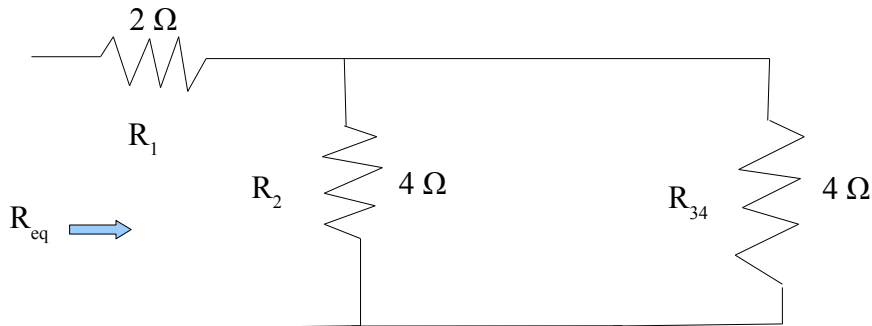
$$R_3 + R_4 = 2\ \Omega + 2\ \Omega = 4\ \Omega$$



Next, we know that  $R_{34}$  and  $R_2$  are in parallel. This produces the equation for their equivalent resistance :
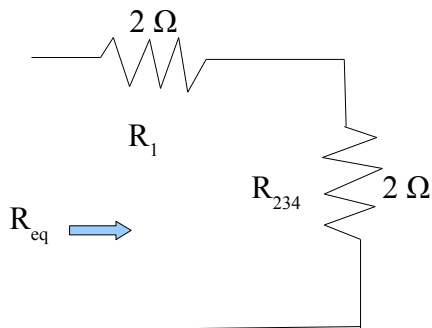
$$(R_{34} * R_2) / (R_{34} + R_2) = (4\ \Omega * 4\ \Omega) / (4\ \Omega + 4\ \Omega) = 16\ \Omega / 8\ \Omega = 2\ \Omega$$




This new circuit gives us our final equation:  $R_1$  and  $R_{234}$  are in series, so :  $R_1 + R_{234} = 2\ \Omega + 2\ \Omega = 4\ \Omega$

This means  $R_{eq}$  equals  $4\ \Omega$ .

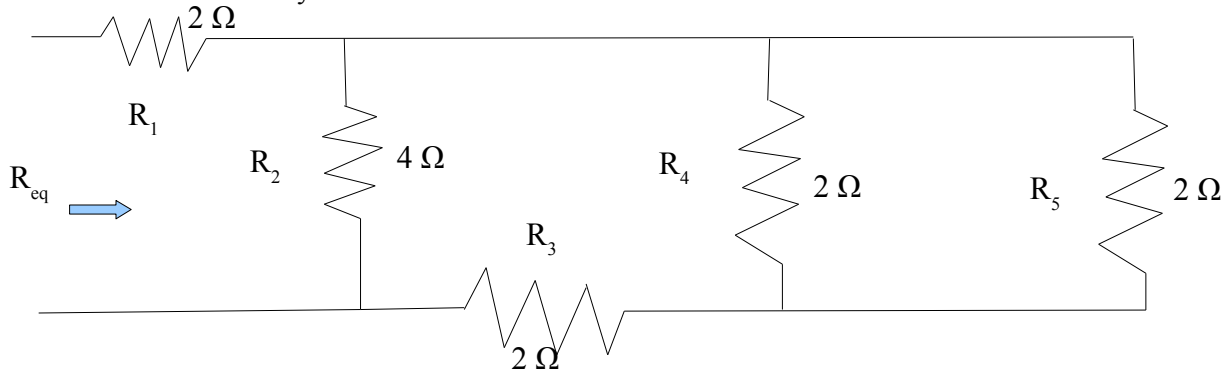
## Problem #1b:

A  $2\Omega$  resistor is placed as a load on this network. Compute the equivalent resistance and explain any changes in the overall resistance that you observe.



In this case,  $R_5$  and  $R_4$  are in parallel. We can find their equivalent resistor with this equation:

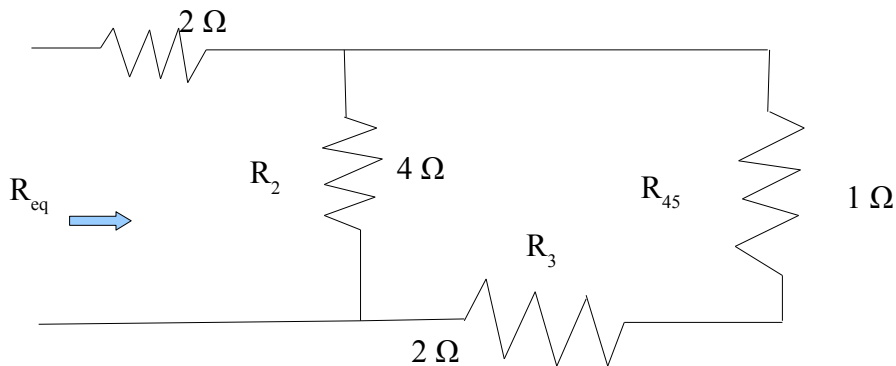
$$(R_5 * R_4) / (R_5 + R_4) = (2\Omega * 2\Omega) / (2\Omega + 2\Omega) = 4\Omega / 4\Omega = 1\Omega$$



From here on out, the circuit is exactly the same as the previous, except  $R_4$  is now  $1\Omega$  instead of  $2\Omega$ . We can therefore use the same equations, substituting the new value, and obtain the new  $R_{eq}$ .

$$R_3 + R_{45} = 2\Omega + 1\Omega = 3\Omega$$
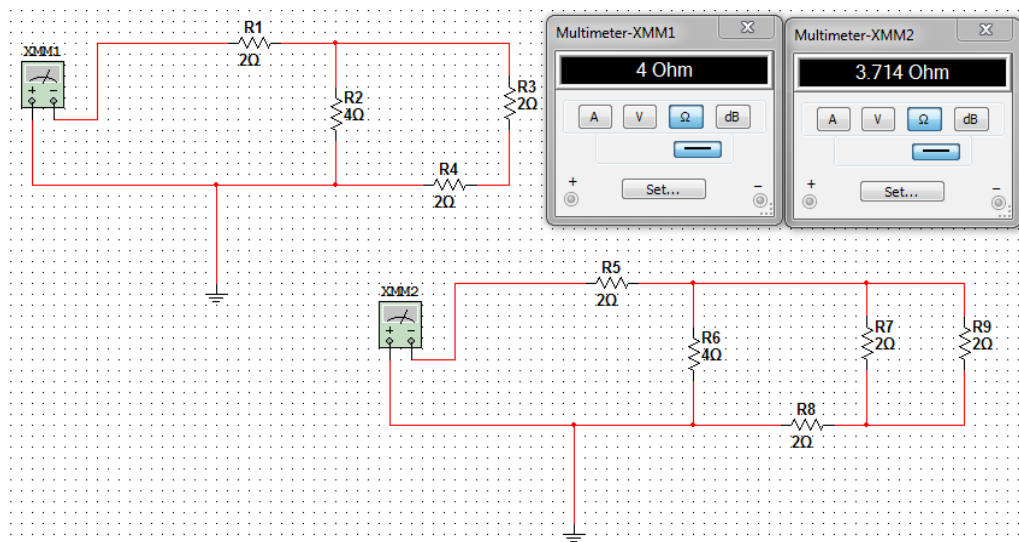
$$(R_{345} * R_2) / (R_{345} + R_2) = (4\Omega * 3\Omega) / (3\Omega + 4\Omega) = 12\Omega / 7\Omega$$




$$R_1 + R_{2345} = 2\Omega + 12/7\Omega = 14/7\Omega + 12/7\Omega = 26/7\Omega = 3.714\Omega$$

Thus, the new  $R_{eq} = 26/7\Omega$ . Our multisim circuit verifies these results:
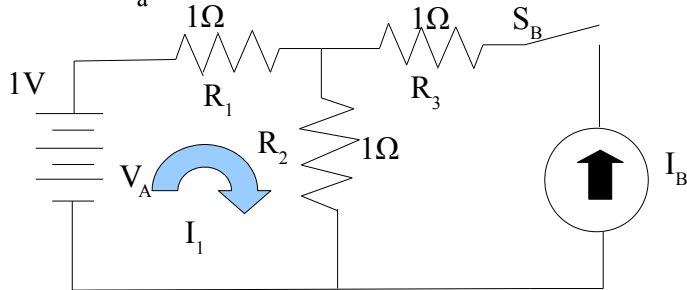
### Problem #2a:

2(a). Set  $V_a = 1\text{VDC}$  and compute the current in the center resistor,  $I_c$ .



Since the switch, SB is open:

$$I_c = I_1$$

Therefore, we can do a KVL around the left inner loop:

$$R_1 * I_1 + R_2 * I_c = 1\text{V}$$

$$1\text{V} = 2I_1$$

$$I_1 = 1/2\text{A}$$


We therefore know that  $I_c = 1/2\text{A}$

We can also analyze the voltages :

$$V = I * R$$

$$V_{R1} = 1\Omega * I_1 = .5\text{V}$$


$$V_{R2} = 1\Omega * I_c = .5\text{V}$$

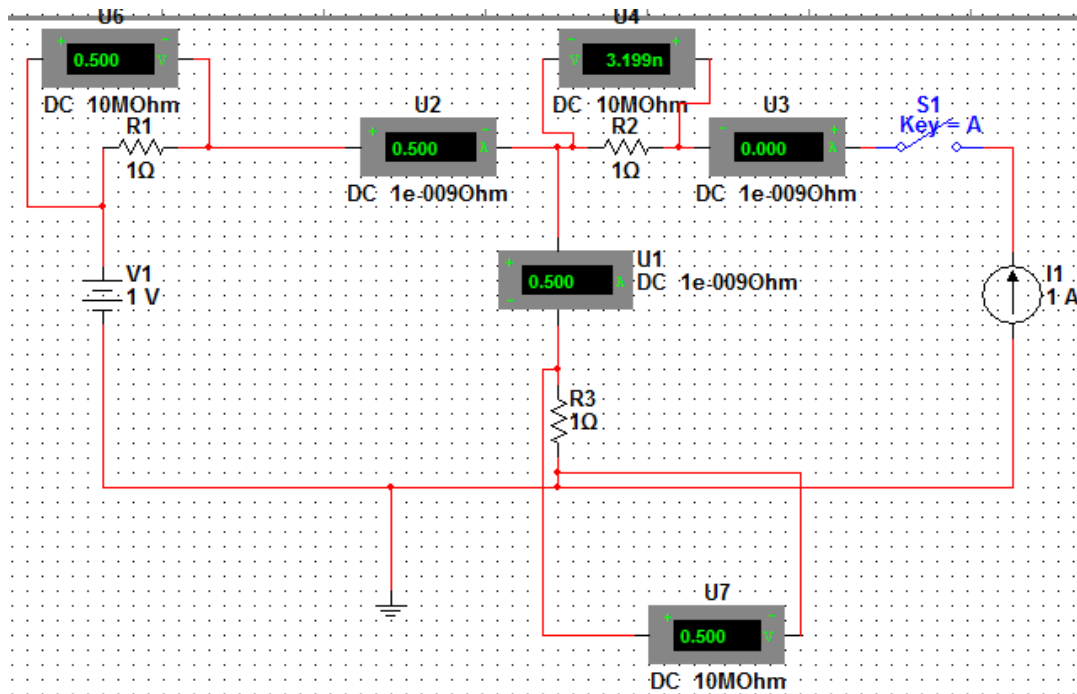

Kirchhoff's voltage law checks out, there is 1V being output by the battery, and .5V is being used by each resistor. The sum of the voltage drops is therefore zero. Multisim confirms this:
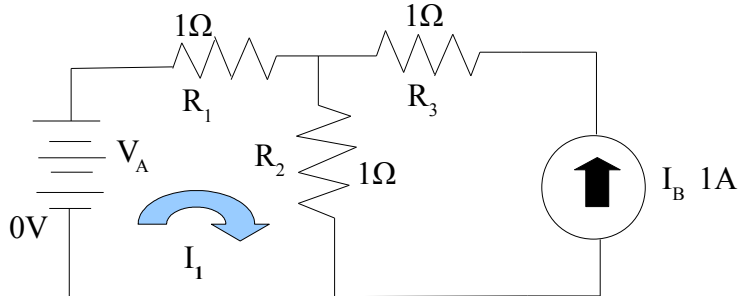
## Problem #2b:

Set  $V_a = 0$  VDC, close the switch  $S_b$ , and set  $I_b = 1$  A. Compute the current in the resistor,  $I_c$ .



Despite  $V_a$  becoming 0, there is still a current,  $I_1$ , running through the circuit along with  $I_B$ . You therefore cannot discount it, like we did with  $I_B$  in the previous part.

$$I_B + I_1 = I_C$$

We will use KVL:

$$I_1 * R_1 - V_A + I_C = 0 \quad I_1 + I_B + I_1 = 0$$

$$2I_1 = -I_B \quad I_1 = -1/2A$$


$$I_B + I_1 = I_C \quad 1A - 1/2A = I_C$$

Thus,  $I_C = 1/2A$ , yet again.

We can find the voltages across the resistors :

$$V_{R3} = I_B * 1\Omega = 1V \quad V_{R1} = I_1 * R_1 = -1/2V \quad V_{R2} = 1\Omega * I_C = 1/2V$$

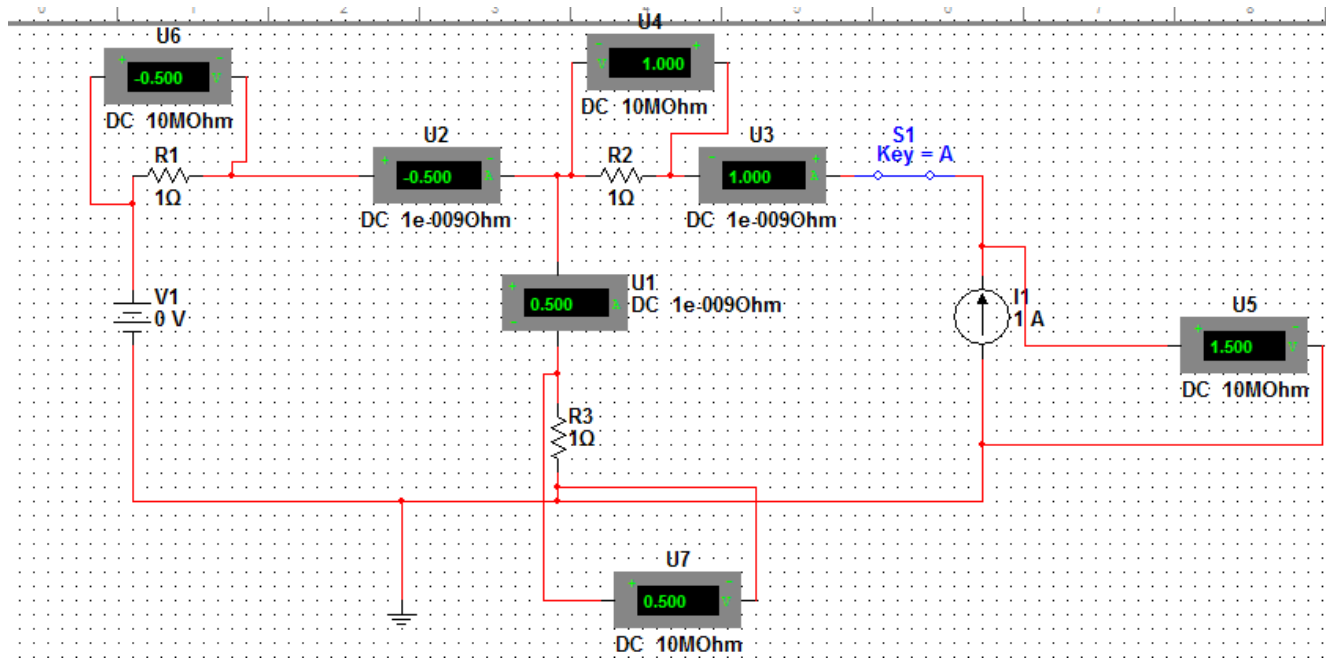Summing up the voltages across either loop will result in the Voltage supplied by  $I_B$ , which is 1.5V.




KCL also holds at the node connecting all the resistors:

$$1A (\text{flowing into the node}) = .5A + .5A (\text{flowing out})$$

Multisim confirms all of this:
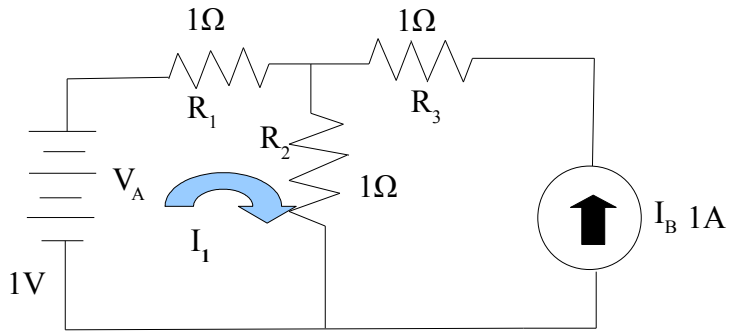
## Problem #2c:

2(c). Set  $V_a = 1\text{VDC}$ , close the switch  $S_b$ , and set  $I_b = 1\text{A}$ . Compute the current in the resistor,  $I_c$ .



We can now do the KVL to get  $I_c$  when both the sources are on:

$$-V_a + I_1 + I_c$$


$$1 = 2I_1 + 1$$

$$I_1 = 0$$

$$I_c = I_1 + I_b = 1\text{A}$$

We can also find the voltages across the resistors:
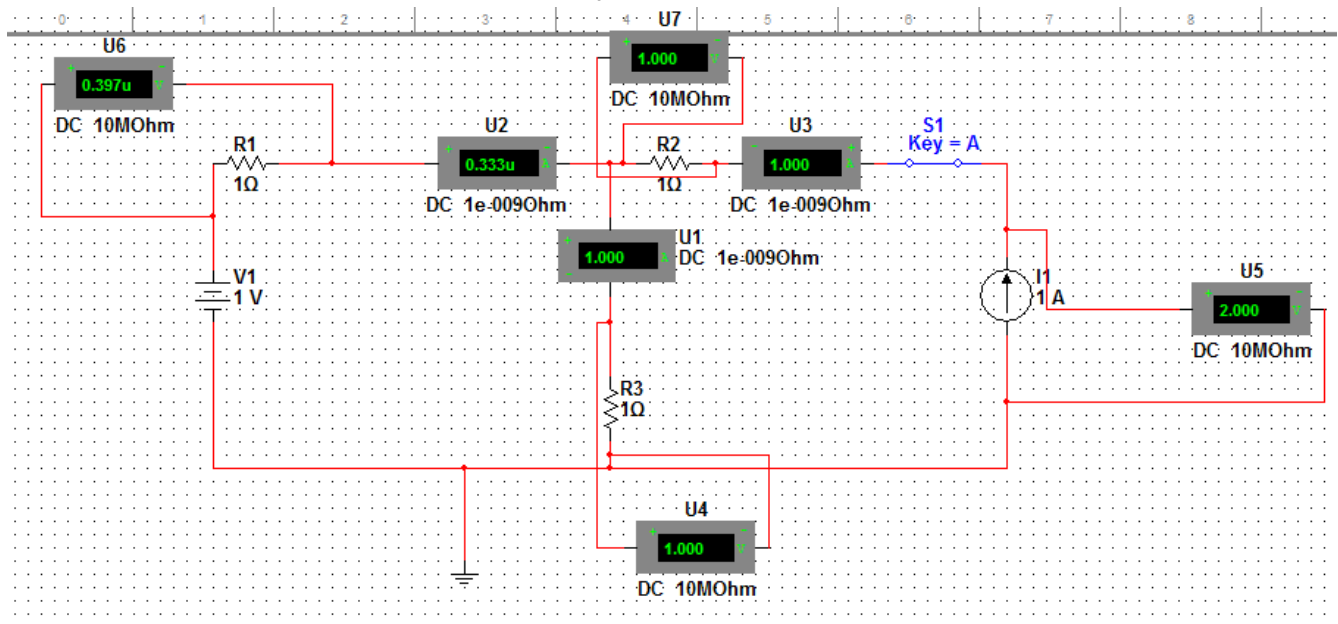
$$V_{R1} = 1\Omega * 0 = 0 \quad V_{R2} = 1\Omega * 1\text{A} = 1\text{V} \quad V_{R3} = 1\Omega * 1\text{A} = 1\text{V}$$



Summing the voltages, we would get that the voltage across the current source would be 2V.

Multisim confirms this:


## Problem #2d:

**2(d).** Does the result of (c) equal the sum of 2(a) and 2(b)? Explain any differences that you observe.

Yes, my result for part c was 1A, and the sum of 2(a) and 2(b) is 1A as well. Why this is the case is simple. Individually, both sources supply  $1/2A$  to the resistor, both in the same direction. It therefore stands to reason that when they're both on, together, they will supply  $1/2A + 1/2A$  to the resistor, or 1A. This may not be true for dependent sources or non-linear elements, but for this circuit, which has neither, it applies perfectly.
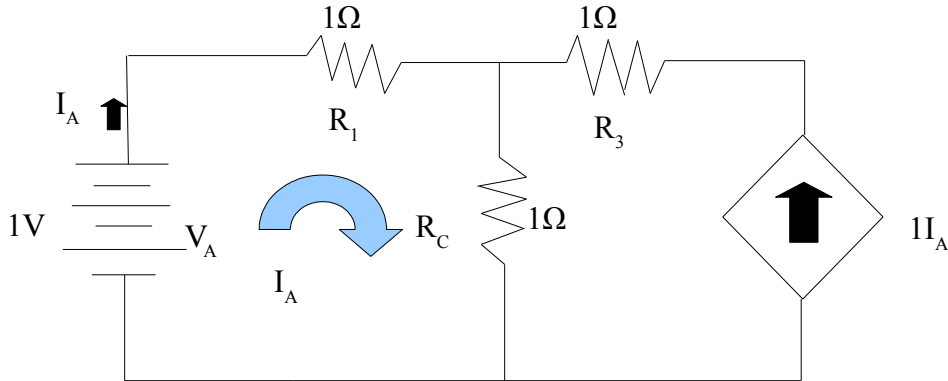
### Problem #3a:

3(a). Compute the power dissipated in  $R_C$ .



This problem is perfectly suited for solving via loop analysis. We can say that the current flowing through the left loop is  $I_A$ , and the right loop is also  $I_A$ . We can write the left loop equation like this:

$$-V_A + I_A * 1\Omega + 1\Omega * (I_A + I_A)$$

Which simplifies to :  $V_A = 3I_A \quad I_A = 1/3A$

Now we can find the power running through  $R_C$

$$P = I^2 R \quad I_{RC} = I_A + I_A = 2I_A = 2/3 \quad P_{RC} = I_{RC}^2 * R_{RC} = (2/3)^2 * 1\Omega = 4/9 \text{ Watts}$$

We can also find the voltage across all of the circuit elements:

$$V_{R1} = I_A * R_1 = 1/3A * 1\Omega = 1/3V \quad V_{RC} = 2I_A * R_C = 2 * 1/3 * 1\Omega = 2/3V$$

$$V_{R3} = I_A * R_3 = 1/3A * 1\Omega = 1/3V$$

To find voltage across the current source, we must do another loop:

$$V_{CS} = I_A * R_3 + 2I_A * R_C = 1/3A * 1\Omega + 2/3A * 1\Omega = 1V$$

If we do any loop, we will find that the sum of the voltages is equal to zero. Furthermore, KCL at the node connecting all three resistors holds true:  $I_A + I_A \text{ Flowing into the node} = 2I_A \text{ Flowing out}$



## Problem #3b:

3(b). Compute the power delivered by the source,  $V_a$ .

The power supplied by the power source is simple:

$$P = V * I$$

$$P_{V_A} = I_A * V_A = 1/3A * -1V = -1/3 \text{ Watts}$$


So the battery is supplying 1/3 Watts of power to the circuit. Likewise, the current source is also supplying 1/3 Watts of power to the circuit.

We should evaluate the power dissipated by all the resistors, because if it does not equal the power supplied by the sources, it means there is an error in the analysis.

$$P_{R_1} = V_{R_1} * I_{R_1} = 1/3V * 1/3A = 1/9 \text{ Watts}$$

$$P_{R_3} = V_{R_3} * I_{R_3} = 1/3V * 1/3A = 1/9 \text{ Watts}$$
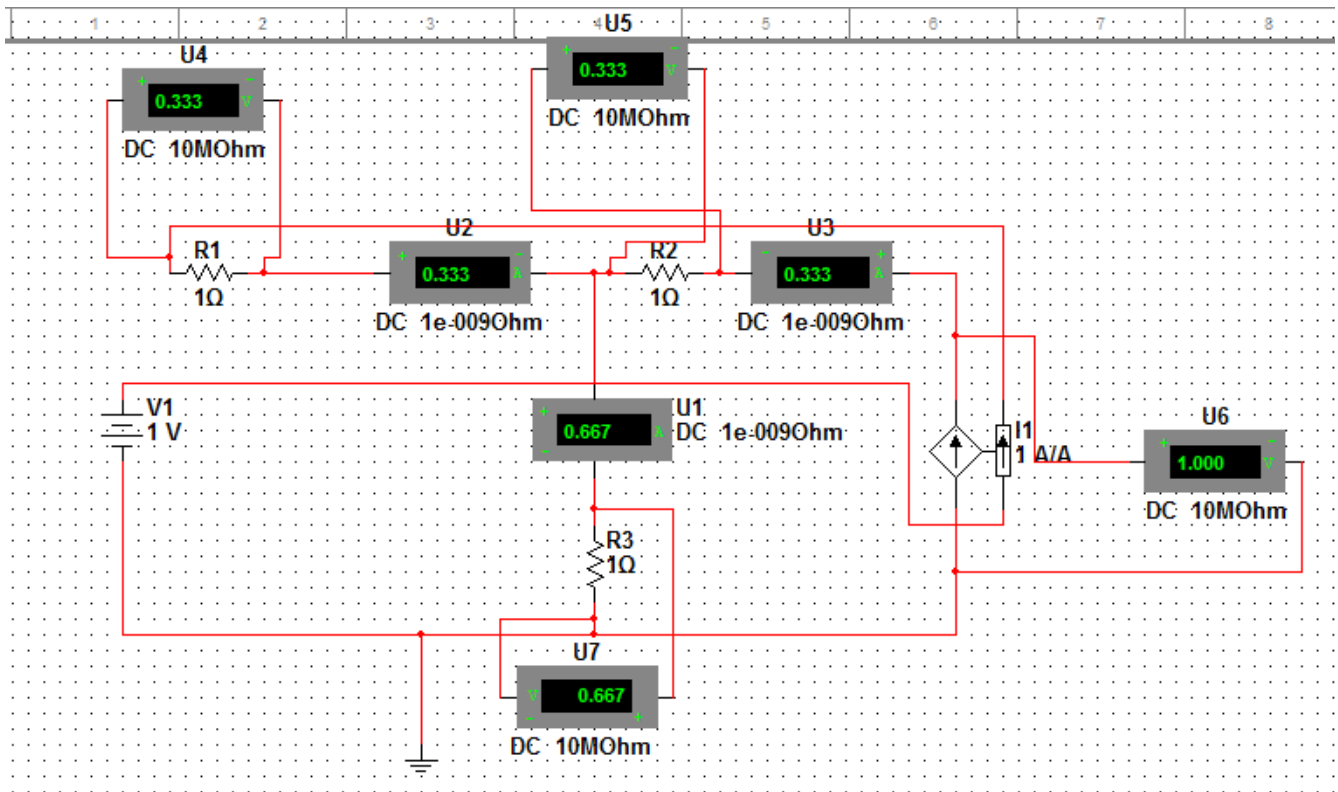
$$P_{R_c} = V_{R_c} * I_{R_c} = 2/3V * 2/3A = 4/9 \text{ Watts}$$



If we add up all the power dissipated by the resistors we get 6/9 Watts dissipated. If we sum up the power supplied by the sources, we get 6/9 Watts supplied. This confirms that our values for power are not incorrect. Multisim Confirms this:

Through multisim, our voltage, current, and power calculations are all validated.