


Vincent Martin  
ECE 2312  
Exam #1 Redo  
9/27/2012

# **Exam 1 Redo**

## Question 1a:
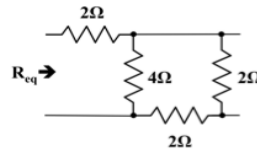
### Problem Description:

Compute the equivalent resistance for the network shown to the right.



### Concepts Used:

I will use the following equations to help solve this.


- $R_{eq\_in\_series} = R1 + R2$
- $R_{eq\_in\_parallel} = \left(\frac{1}{R1} + \frac{1}{R2}\right)^{-1}$

### My Work:

1. Combine the two 2 Ohm resistors on the right in series by  $2 + 2 = 4$  to give circuit as seen in Multi-sim step 2.
2. We now have two 4 Ohm resistors in parallel. We now use our parallel equation of  $\left(\frac{1}{4} + \frac{1}{4}\right)^{-1} = 2 \text{ Ohm}$  to give us the circuit as seen in Multi-sim step 3.
3. Finally, we are left with the two remaining resistors in series. We then add then up  $2+2=4$  to give us a final equivalent resistance of 4 Ohms.
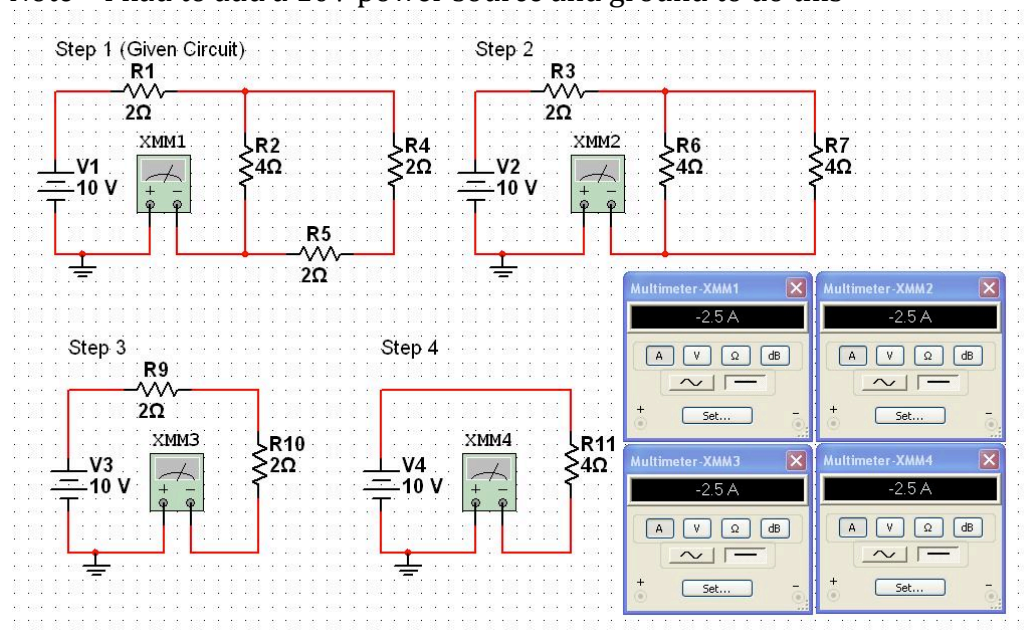
### Multi-sim Work:

Note - I had to add a 10V power source and ground to do this



Conclusion:


Equivalent resistance = 4 Ohm.

It can be seen that the current is identical in each step of my Multi-sim simulation. If this were not the case then my

## Question 1b:
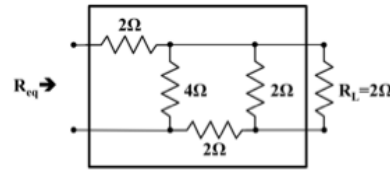
### Problem Description:

1(b). A  $2\Omega$  resistor is placed as a load on this network. Compute the equivalent resistance and explain any changes in the overall resistance that you observe.



### Concepts Used:

I will use the following equations to help solve this.


- $R_{eq\_in\_series} = R1 + R2$
- $R_{eq\_in\_parallel} = \left(\frac{1}{R1} + \frac{1}{R2}\right)^{-1}$

### My Work:

1. Add the two resistors on the right in parallel to get  $\left(\frac{1}{2} + \frac{1}{2}\right)^{-1} = 1\text{ Ohm}$  as seen in step 1 of the Multi-sim diagram.
2. Add the 1 Ohm and 2 Ohm resistor in series  $1 + 2 = 3$  to get 3 Ohm as seen in step 2 of the Multi-sim diagram.
3. Add the 3 Ohm and 4 Ohm resistors in parallel to get  $\left(\frac{1}{3} + \frac{1}{4}\right)^{-1} = 12/7\text{ Ohm}$  as seen in step 3 of the Multi-sim diagram.
4. Add the  $12/7$  Ohm and 2 Ohm resistor in series to get  $26/7\text{ Ohm}$ .
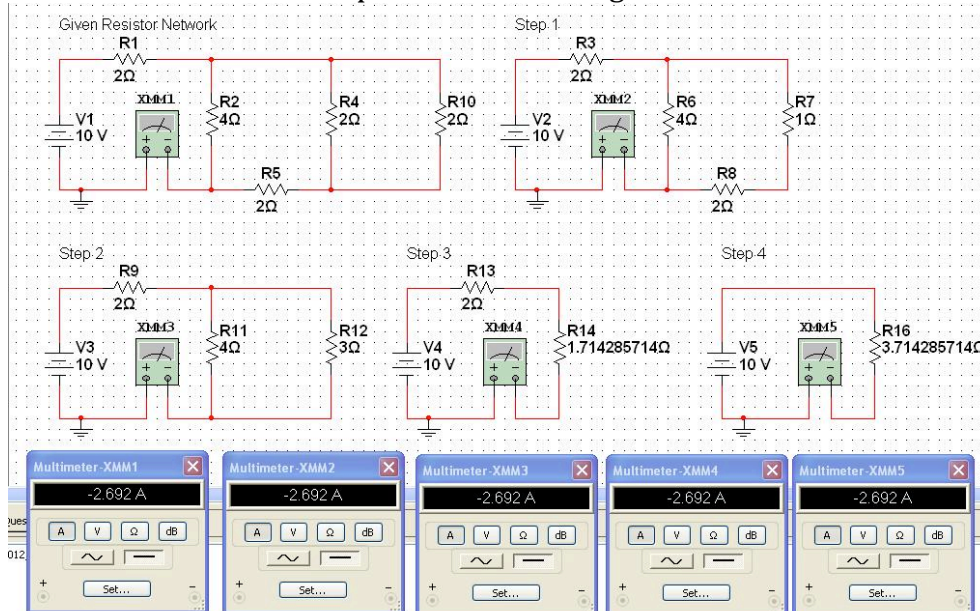
### Multi-sim Work:

Note – I had to add a 10V power source and ground to do this.



Conclusion:

Equivalent resistance =  $26/7$  Ohm.


It can be seen that the current is identical in each step of my Multi-sim simulation. If this were not the case then my

## Question 2a:

### Problem Description:

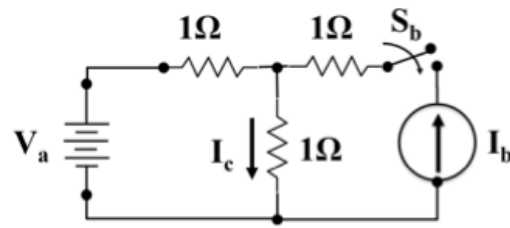2. Consider the circuit shown to the right.

2(a). Set  $V_a = 1$  VDC and compute the current in the center resistor,  $I_c$ .



### Concepts Used:

In this problem I will use KVL to solve. KVL states that all voltages in a loop must add up to 0.

$$V = IR$$

It is important to note that **THE SWITCH IS OPEN**, ergo we can ignore the  $I_b$  current source and the 1 Ohm resistor in that portion of the circuit.

### My Work:


To do KVL we start at the  $V_a$  source and continue clockwise through the circuit. Substituting the voltages for the resistor as  $I_c \cdot \text{Resistor}$  we can then solve for our unknown  $I_c$ .

$$V_a - \text{Voltage at 1}^{\text{st}} \text{ 1 Ohm Resistor} - \text{Voltage at 2}^{\text{nd}} \text{ 1 Ohm Resistor} = 0$$

$$1 - (1 \text{ Ohm} \cdot I_c) - (1 \text{ Ohm} \cdot I_c) = 0$$

$$I_c = 1/2$$

### Multi-sim Work:

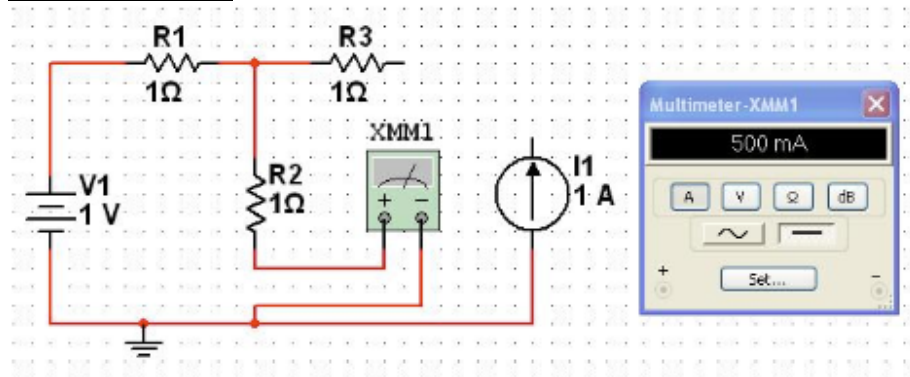

### Conclusion:


$$I_c = \frac{1}{2} \text{ A}$$

This is verified as seen above in my Multi-sim simulation.

### Question 2b:
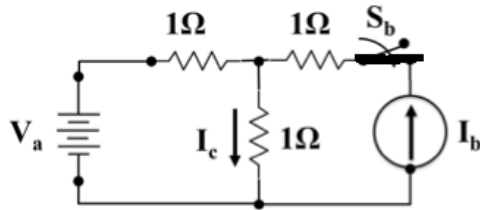
#### Problem Description:

Set  $V_a = 0$  VDC, close the switch  $S_b$  and set  $I_b = 1$  A.  
Compute the current in the resistor  $I_c$ .




#### Concepts Used:

In this problem I will use nodal analysis to calculate nodal voltages  $V_1$  and  $V_2$  as seen in the below picture.

It is important to note that **THE SWITCH IS CLOSED**. Also,  $V_a$  is set to 0, so we can essentially ignore it in our calculations.
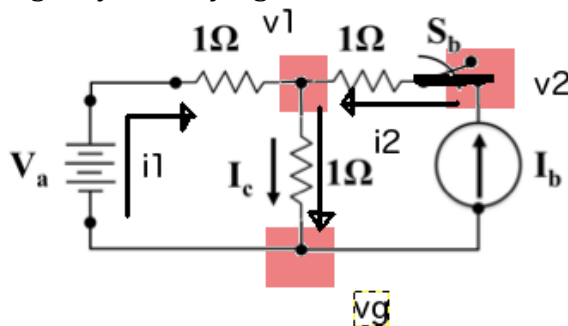
#### My Work:

I begin by identifying the nodes in the circuit,  $v_1$ ,  $v_2$  and  $v_g$  (ground).



Secondly, I identify current names and direction.  $I_1$ ,  $I_c$ ,  $I_2$  and  $I_b$ .

Third, I setup KCL equations for each of the identified nodes.

$$\mathbf{V1: } I_1 + I_2 = I_c$$

$$\mathbf{V2: } I_b = I_2$$

**Vg:**

$$I_b + I_1 = I_c \rightarrow I_2 + I_1 = I_g$$

Identify the equation for each current.

$$I_1 = (V_g - V_1)/1$$

$$I_2 = (V_2 - V_1)/1$$

$$I_c = (V_1 - V_g)/1$$

$$I_b = 1$$

Now that we know the equations for the currents we then put them into our equations for our KCL. This will allow us to solve for the unknown  $V_1$  voltage and will finally allow us to determine the current  $I_c$ .

**V1:**

$$(V_g - V_1) / 1 + (V_2 - V_1) / 1 = (V_1 - V_g) / 1$$


**V2:**

$$(I_b = I_2)$$

$$1 = (V_2 - V_1) / 1$$

We are left with 2 equations and 2 unknowns. Solving for  $V_1$  we get  $V_1 = 1/2$  volt. Putting  $1/2$  volt into our equations for  $I_c$  will allow us to solve for  $I_c$ .

Multi-sim Work:

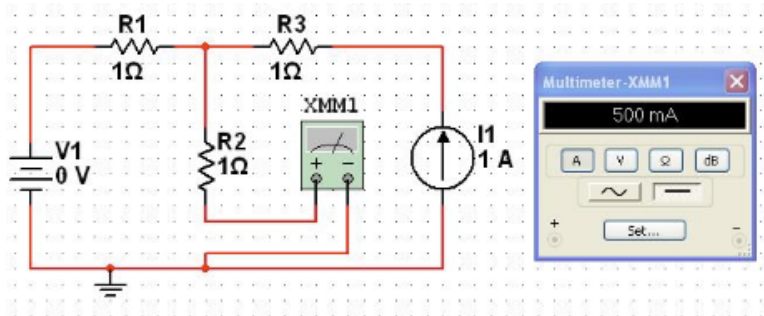

Conclusion:

$$V_1 = 1/2$$

Putting  $V_1$  into  $I_c = (V_1 - V_g)/1$  gets us...


$$I_c = 1/2 \text{ A}$$

This is verified as seen above in my Multi-sim simulation.



## Question 2c and d:

### Problem Description:

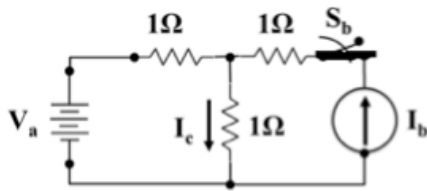


Set  $V_a = 1$  VDC, close the switch  $S_b$ , and set  $I_b = 1$  A. Compute the current in the resistor,  $I_c$ .

### Concepts Used:

To solve this circuit we will need the voltage going through the path  $I_c$  travels. In order to do this we will use nodal analysis and KCL.
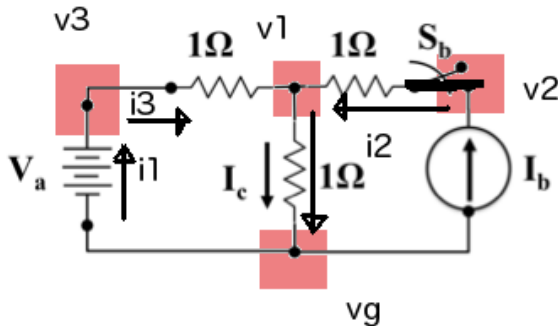
### My Work:

I begin by identifying the nodes in the circuit,  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_g$  (ground).



Secondly I label currents  $I_1$ ,  $I_2$ ,  $I_b$  and  $I_c$  and their direction.

Third, I identify the equations for each current.

$$i_1 = ???$$

$$i_3 = (v_3 - v_1)/1$$

$$i_2 = (v_2 - v_1)/1$$

$$i_c = (v_1 - V_g)/1$$

$$i_b = 1$$

Fourth, I can then determine my KCL equations for each node  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_g$  and then substitute the current equations in so that I can solve for  $I_c$ .

### V1:

$$i_2 + i_3 = i_c$$

$$\frac{v_2 - v_1}{1} + \frac{v_3 - v_1}{1} = \frac{v_1 - v_g}{1}$$

**V2:**

$$i2 = ib$$

$$\frac{v2 - v1}{1} = 1$$

**V3:**

$$i1 = i3$$

$$i1 = \frac{v3 - v1}{1}$$

**Vg:**

$$ib + i1 = ic$$


$$1 + i1 = \frac{v1 - vg}{1}$$

To find  $v1$  we will have to use the equations for the nodal voltage at  $V1$  and  $V2$  and the fact that  $v3 = 1v$ . Doing so will give us two equations with two unknowns.

Solving for  $V1$  gives us a voltage of 1.

This voltage can then be put into our equation for  $Ic$  to get a current of 1A.

Multi-sim Work:

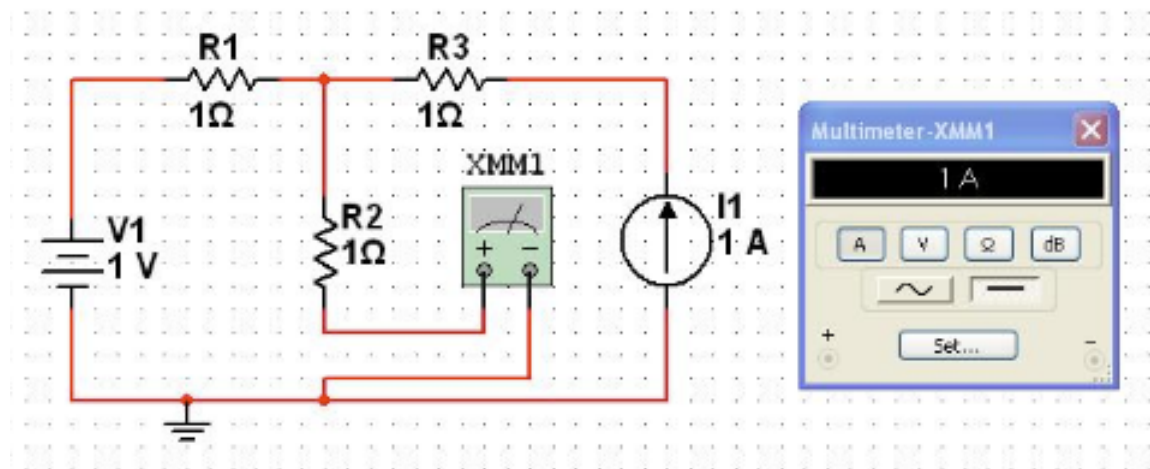

Conclusion:

It can be seen that Multi-sim matches with my calculated answer. Therefore it can be said that my answer is correct.


It can also be seen that our previous two answers are the same. It is because each previous problem basically represents both sides of the circuit. Conservation of energy states that these would both add up to be double due to both of them being equal to each other.

### Question 3a:

#### Problem Description:

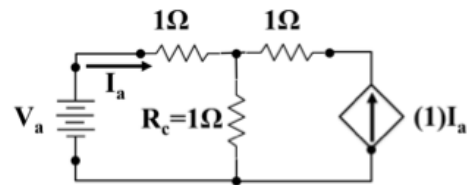3. For the circuit shown to the right, assume  $V_a = 1$  VDC:

3(a). Compute the power dissipated in  $R_c$ .




#### Concepts Used:

To solve this circuit we will need the voltage and current going through the  $R_c$  resistor and use that to calculate power with  $P = IV$  or  $V^2/R$ .
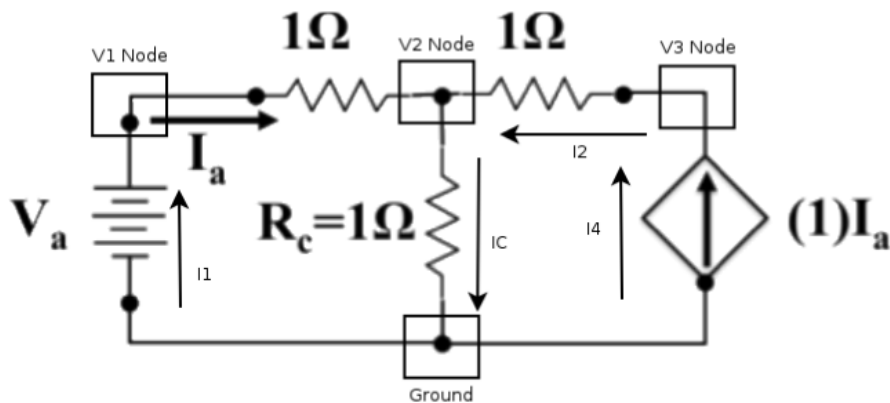
#### My Work:

I begin by identifying the nodes in the circuit,  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_g$  (ground).

Secondly I label currents  $I_1$ ,  $I_2$  and  $I_c$  and their direction.



Third, I identify the equations for each current.

$$i_1 = ???$$

$$i_a = (v_1 - v_2)/1$$

$$i_2 = (v_3 - v_2)/1$$

$$i_c = (v_2 - V_g)/1$$

$$i_4 = i_a = (v_1 - v_2)/1$$

Also note that  $V_1 = 1$  v.

I can then determine my KCL equations for each node  $v_1$ ,  $v_2$  and  $v_3$  and then substitute the current equations in so that I can solve for  $V_2$  and the current through  $R_c$ .

#### V1:

$$i_1 = i_a$$

$$i_1 = 1 - v_2$$

**$\Omega V2$ :**

$$i_a + i_3 = i_c$$
$$3v_2 - v_3 = 1$$

**V3:**

$$i_4 = i_3$$
$$1 = v_3$$

Using the systems of equations above for V2 and V3 I can then solve for v2 and determine that...


$$V_2 = 2/3 \text{ V}$$


$$i_c = (v_2 - V_g)/1$$
$$i_c = (\frac{2}{3} - 0)/1 = 2/3 \text{ A.}$$

Now that we have v2 and ic we can then use  $P = IV$  to determine that

$$P = (2/3) * (2/3) = 4/3 \text{ W.}$$

Multi-sim Work:

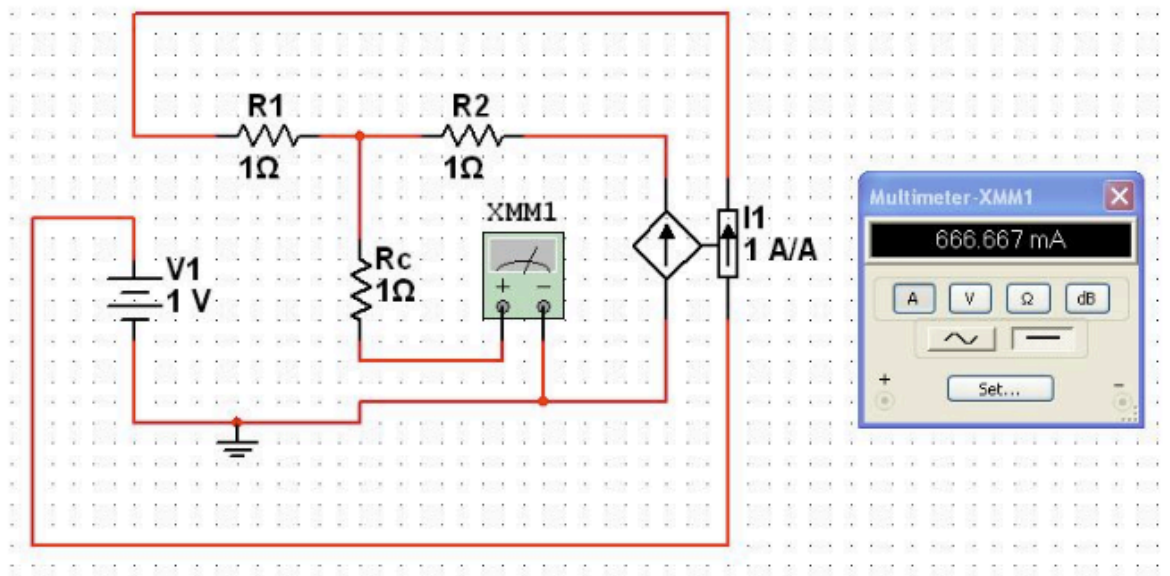

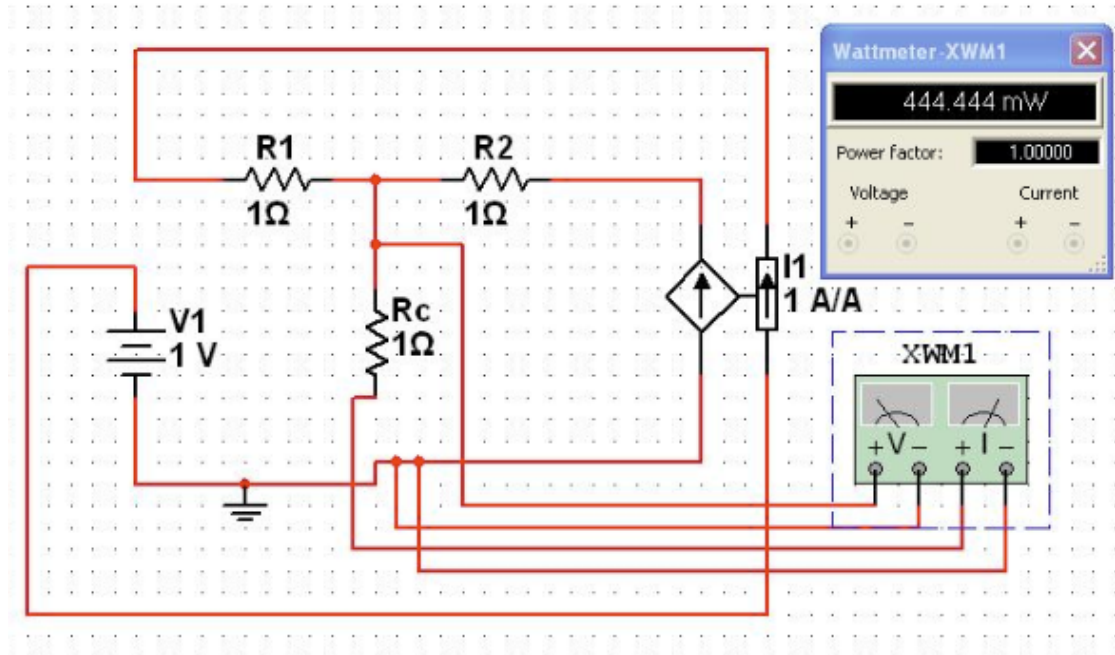

Conclusion:

My worked results and Multi-sim both verify that the following answers are correct.

$$V2 = 2/3 \text{ V}$$

$$i_c = (v2 - Vg)/1$$

$$i_c = \left(\frac{2}{3} - 0\right)/1 = 2/3\text{A.}$$


$$P = (2/3)*(2/3) = 4/3 \text{ W.}$$

### Question 3b:

#### Problem Description:

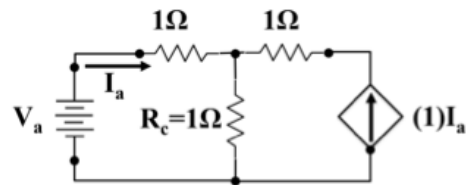3. For the circuit shown to the right, assume  $V_a = 1$  VDC:

3(a). Compute the power dissipated in  $R_c$ .




#### Concepts Used:

To solve this circuit we will need the voltage and current going through  $V_a$  and use that to calculate power with  $P = IV$  or  $V^2/R$ .
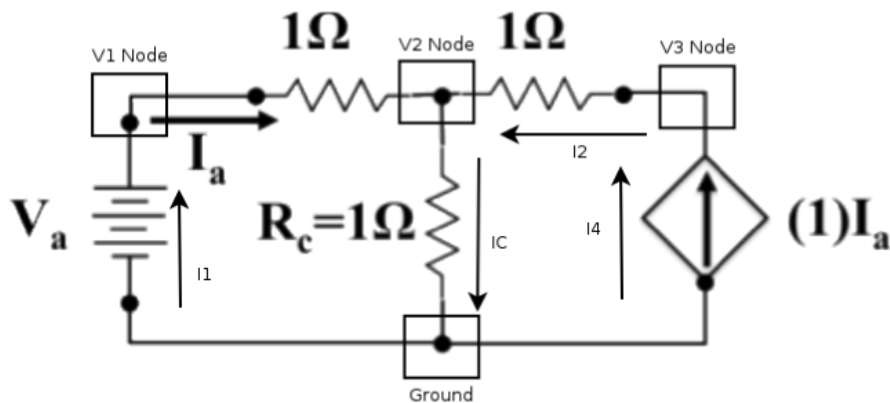
#### My Work:

I begin by identifying the nodes in the circuit,  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_g$  (ground).

Secondly I label currents  $I_1$ ,  $I_2$  and  $I_c$  and their direction.



Third, I identify the equations for each current.

$$i_1 = ???$$

$$i_a = (v_1 - v_2)/1$$

$$i_2 = (v_3 - v_2)/1$$

$$i_c = (v_2 - V_g)/1$$

$$i_4 = i_a = (v_1 - v_2)/1$$

Also note that  $V_1 = 1$  v.

I can then determine my KCL equations for each node  $v_1$ ,  $v_2$  and  $v_3$  and then substitute the current equations in so that I can solve for  $V_2$  and the current through  $R_c$ .

#### V1:

$$i_1 = i_a$$

$$i_1 = 1 - v_2$$

**V2:**

$$i_a + i_3 = i_c$$
$$3v_2 - v_3 = 1$$

**V3:**

$$i_4 = i_3$$
$$1 = v_3$$

Using the systems of equations above for V2 and V3 I can then solve for  $v_2$  and determine that...

$$V_2 = 2/3 \text{ V}$$

Now that we know that  $V_2 = 2/3v$  we can then use  $V_2$  in our equation for the  $V_1$  node to determine that  $i_a$

$$i_1 = 1 - 2/3 = 1/3A.$$


Now that we have  $v_1$  and  $i_1$  we can then use  $P = IV$  to determine that

$$i_a = (v_1 - v_2)/1$$
$$i_a = \frac{1 - \frac{2}{3}}{1} = 1/3A$$

With this we know that  $i_1 = 1/3$  and can determine the power output with the equation found below.

$$P = (1/3) * (1) = 1/3W.$$

Multi-sim Work:

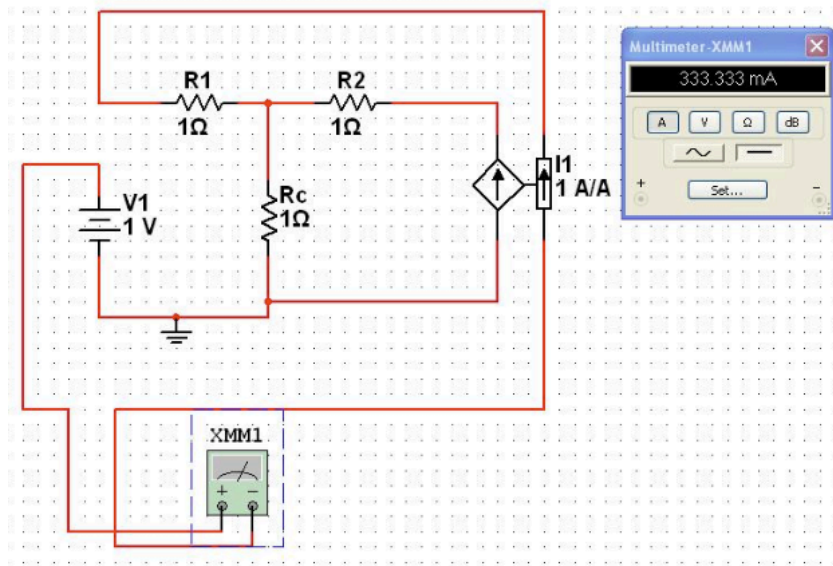



Conclusion:

My worked results and Multi-sim both verify that the following answers are correct.

$$V_2 = 2/3 \text{ V}$$

$$i_a = \frac{1 - \frac{2}{3}}{1} = 1/3 \text{ A}$$

With this we know that  $i_1 = 1/3$  and can determine the power output with the equation found below.

$$P = (1/3) * (1) = 1/3 \text{ W.}$$