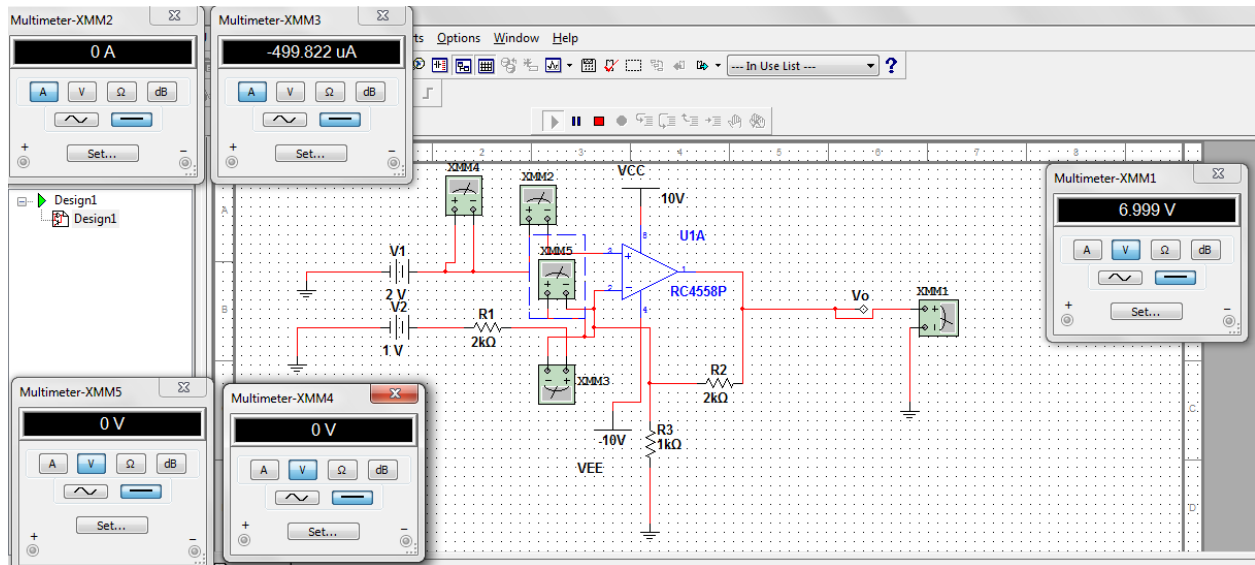


Dennis Chong

Exam 2 Redo

Question 1



Let the node connecting R_1 , R_2 and R_3 be V

For an ideal op-amp, $I^- = I^+ = 0$ and $V_1 = V_2$

KCL @ Node V (Nodal analysis)

$$V/1 + (V-V_0)/2 + (V-V_2)/2 + I_2 = 0$$

$$V_1/1 + (V_1-V_0)/2 + (V_1-V_2)/2 = 0$$


$$2V_1 + V_1 - V_0 + V_1 - V_2 = 0$$

$$V_0 = 4V_1 - V_2$$

As a test, I set V_1 and V_2 to be 2V and 1V respectively on multisim. As shown in the above, I obtained V_0 as 7V, justifying the equation $V_0 = 4V_1 - V_2$

Question 2

For the first part, open current source.

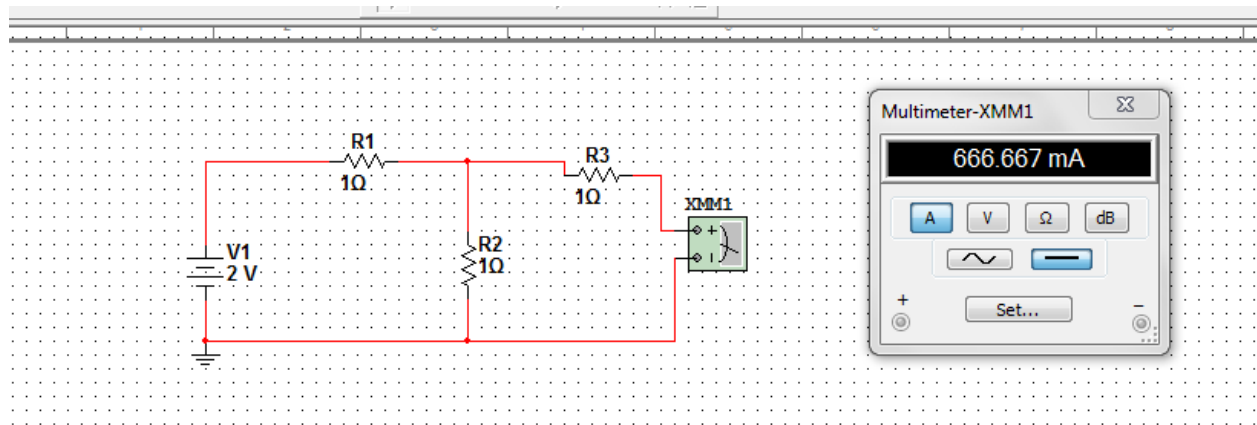

Let I_o be the total current.

$$R_{\text{total}} = 1 + (1 \parallel 1) = 1.5 \text{ ohms}$$

$$I_o = V_s / R_{\text{total}}$$


$$I_o = 2 / (1.5) = 2/3 \text{ A}$$

$$R_L = R_{\text{th}} = 1.5 \text{ ohms}$$

$$P'_L = (2/3)^2 * (3/2) = 2/3 \text{ W}$$

For the second part,

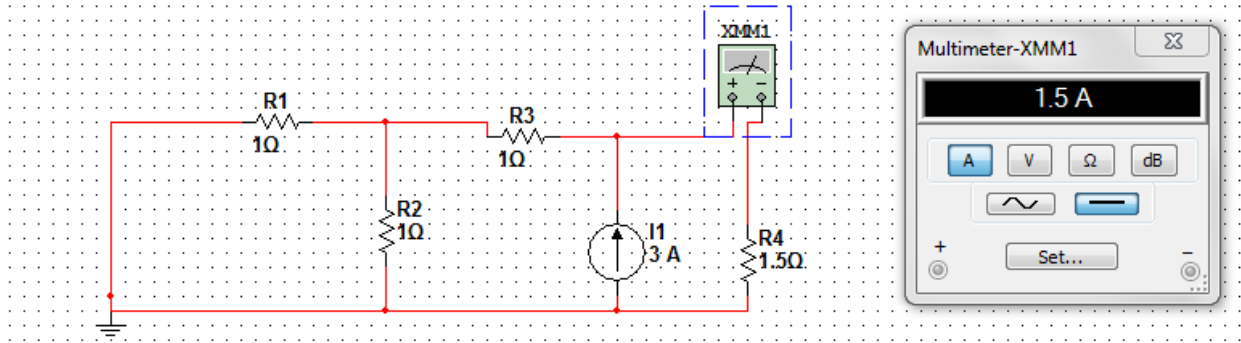Short the voltage source, circuit becomes



$$R_L = R_{th} = 1.5\text{ohms}$$

Let I_{sc} be the current flowing through the branch on the furthest right.

Since the resistance on the left and right side of the current source is equal, therefore the current is equally split between both the branches.

$$I_{sc} = 3/2 = 1.5\text{A}$$

$$P''_L = (3/2)^2 * (3/2)$$


$$P''_L = 27/8 \text{ W}$$

Therefore, total power is

$$P_o = P'_L + P''_L = 2/3 + 27/8$$


$$P_o = 97/24 \text{ W}$$

Question 3

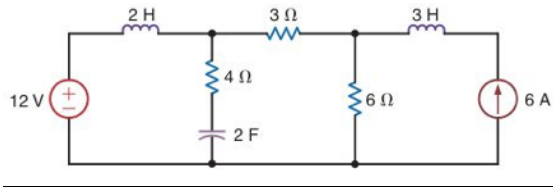

The first step to this problem is to have the inductors be short circuit and capacitors to be open circuit.

The circuit should turn out like below.

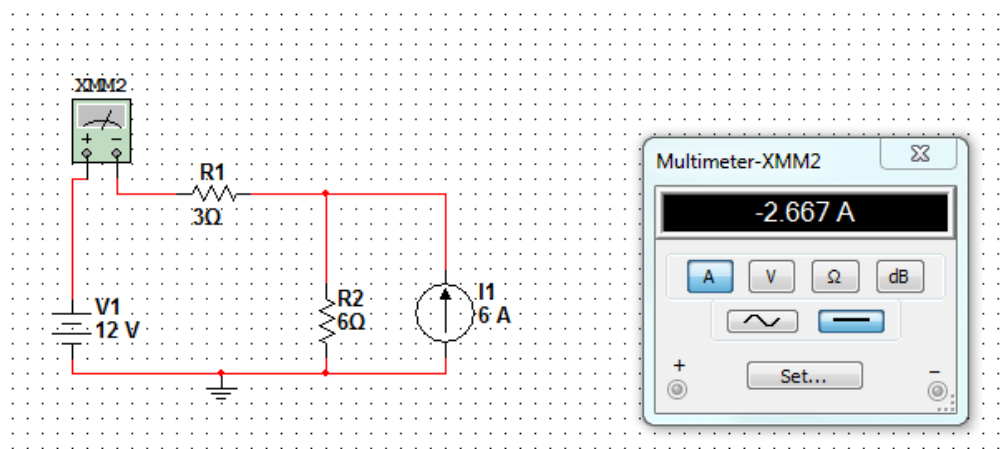

There are two methods to calculate the current across the 3ohms resistor, the mesh and nodal analysis.

Mesh Analysis

Let I_1 = the current flowing in the left loop

$$I_2 = 6A$$

KVL @ left loop

$$-12 + 3I_1 + 6(I_1 + I_2) = 0$$

$$3I_1 + 6I_1 + 36 = 12$$

$$I_1 = -8/3 = -2.667A$$

Since $P = I^2R$,

$$\text{Therefore, Power across 3ohms: } P_{3\text{ohms}} = (-8/3)^2 * (3) = 64/9 \text{ W}$$

Nodal Analysis

Let V_2 be the middle node and V_1 be at the left node.

Note that $V_1 = 12V$

$$(V_2 - V_1)/3 - 6 + V_2/6 = 0$$

$$(V_2 - V_1)/3 + V_2/6 = 6$$

$$2(V_2 - V_1) + V_2 = 36$$

$$3V_2 - 2V_1 = 36$$

$$V_2 = 20$$

$V_o = V_1 - V_2 = -8V$ (Current flowing from right to left across the 3ohms resistor)

$$I_{3ohms} = V_o/R_1 = 8/3A$$

Since $P = I^2R$,

Therefore, Power across 3ohms: $P_{3ohms} = (8/3)^2 * (3) = 64/9 W$

(The above set of workings function as a prove that I am able to find Power and Current across each device)

For 3H inductor

We know that a current of 6A is flowing through the inductor.

The formula of energy dissipation of an inductor is given as

$$E = 1/2L(I^2)$$

$$E = 1/2(3)(36) = 54W$$

For 2F Capacitor

We know that the Voltage across the branch with capacitor is parallel to the V_{source} on the left.

$$V_c = V_{source} = 12V$$

Dissipation of energy of a capacitor is $1/2CV^2$

$$E = 1/2(2)(144) = 144W$$

