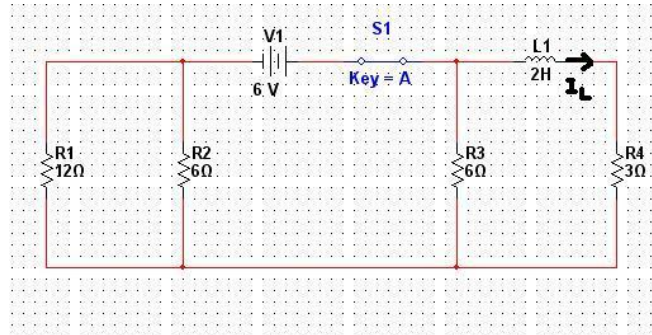


Saurav Guru


Exam 3 Rework

Problem 1: Find the current $I_L(t)$



$$I_L(t) = K_1 + K_2 e^{(-t/T)}$$

At $t = 0^-$

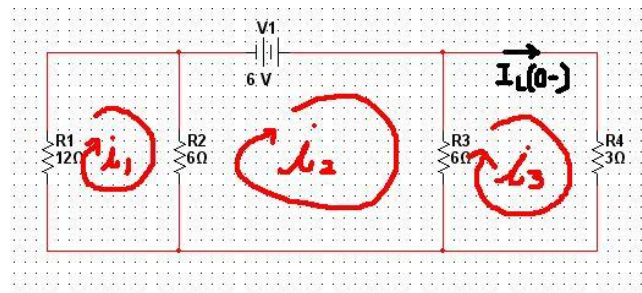

Do KVL

$$12i_1 + 6i_1 - 6i_2 = 0$$

$$3i_1 - i_2 = 0$$

$$6i_2 - 6i_1 + 6i_2 - 6i_3 = 6$$

$$-i_1 + 2i_2 - i_3 = 1$$

$$6i_3 - 6i_2 + 3i_3 = 0$$


$$-2i_2 + 3i_3 = 0$$

Use Matlab to find i_1 , i_2 , and i_3 .

$$i_1 = 0.33 A \quad i_2 = 1 A$$

$$i_3 = 0.67 A = I_L(0-) = I_L(0+)$$

At $t = \text{infinity}$

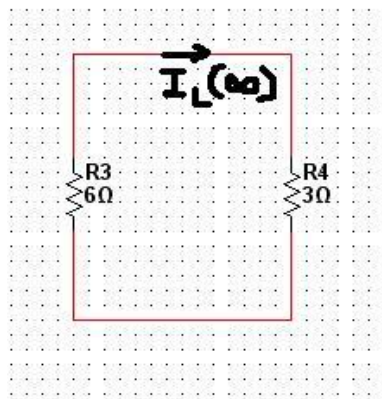

$$I_L(\text{infinity}) = 0 A$$

Find the constants K_1 and K_2 .


$$I_L(\text{infinity}) = 0 = K_1$$

$$I_L(0+) = K_1 + K_2$$

$$0.67 = K_1 + K_2$$

$$K_2 = 0.67$$

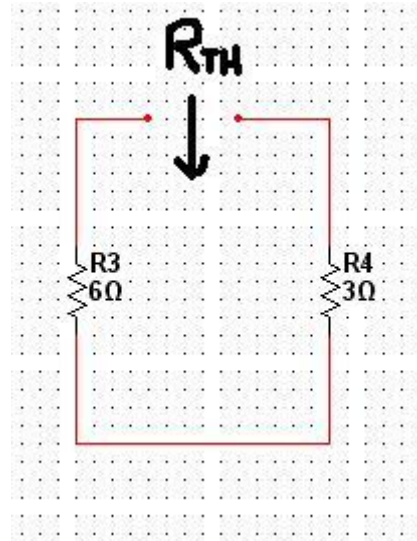To find the time constant (T), first find the R Thevenin and then used $T = L/R_{th}$ to find the time constant.



$$R_{TH} = 6 + 3 = 9 \text{ ohms}$$


$$T = L / R_{TH} = 2 / 9 = 0.22 \text{ s}$$

Now we can combine everything to get the final answer.


$$I_L(t) = 0.67 e^{(-t/0.22)} \text{ A} \quad \text{OR} \quad I_L(t) = 0.67 e^{(-4.5t)} \text{ A}$$

Multisim Result for $i_L(t)$:


At $t = 0^-$

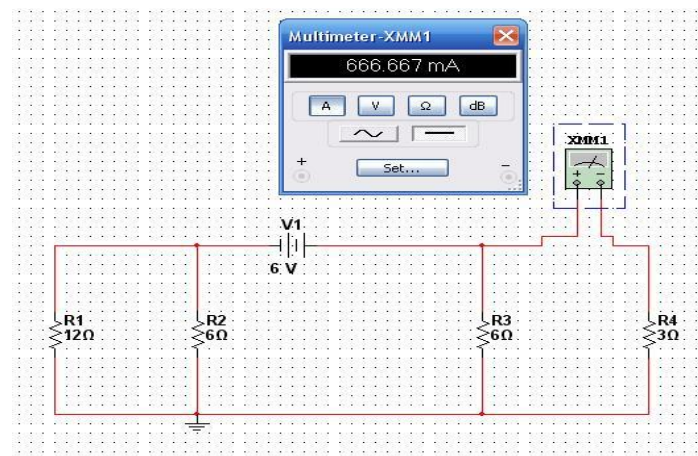


At $t = \infty$

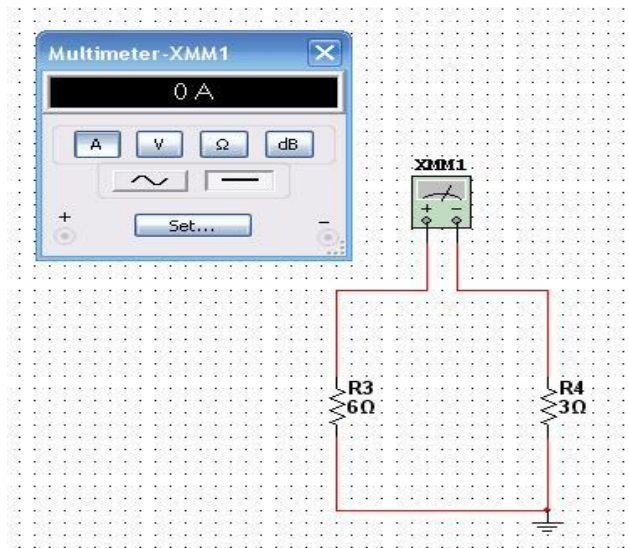

Final result:

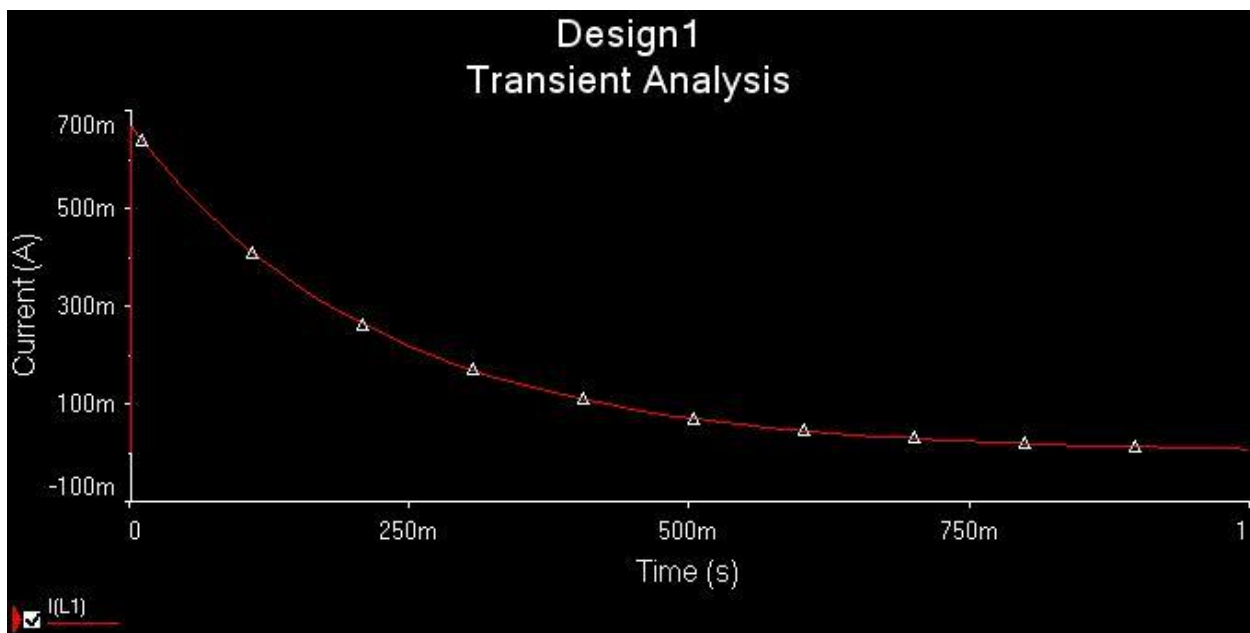

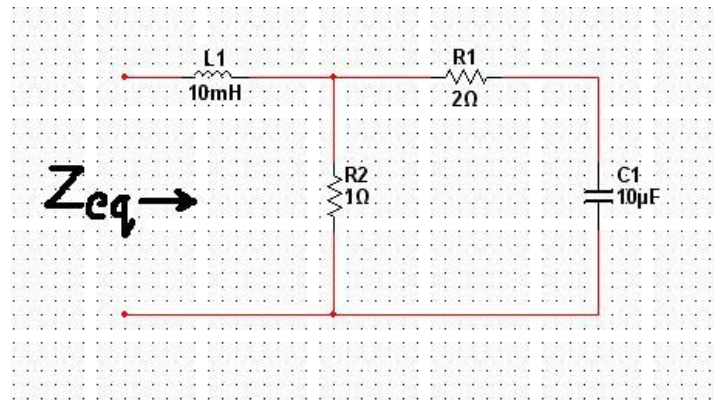Problem 2: Find the equivalent input impedance assuming a frequency of 60 Hz



$$Z_L = j\omega L = j(377)(10 \cdot 10^{-3}) = j3.77 \text{ ohms}$$

$$Z_C = -j/\omega C = -j(1/(377)(10 \cdot 10^{-6})) = -j265.25 \text{ ohms}$$

$C1$ is in series with $R1$:

$$-j265.25 + 2 = 2 - j265.25 \text{ ohms}$$

$(C1 + R1)$ is parallel with $R2$:


$$2 - j265.25 \parallel 1 = 1 - j0.0038 \text{ ohms}$$

$((C1 + R1) \parallel R2)$ is in series with $L1$:

$$1 - j0.0038 + j3.77 = 1 + j3.77 \text{ ohms}$$

$$Z_{eq} = 1 + j3.77 \text{ ohms}$$

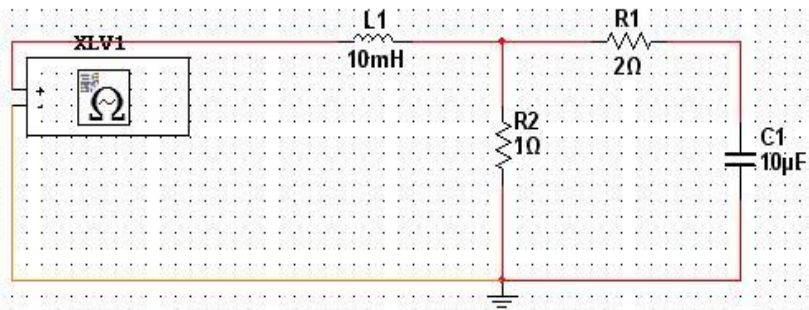Multisim Result for equivalent Impedance:



Impedance Meter -XLV1

Frequency Sweep

Start: 60
Stop: 60


Output Options

Number of Points: 1
Scale Type: Linear

<i>f (Hz)</i>	<i>R (ohm)</i>	<i>X (ohm)</i>	<i> Z (ohm)</i>	?
60	-49	3.76614	49.1446	↑
0	0	0	0	
0	0	0	0	
0	0	0	0	
0	0	0	0	
0	0	0	0	↓

Clear Data when Simulation Starts

Problem 3: Find V_x

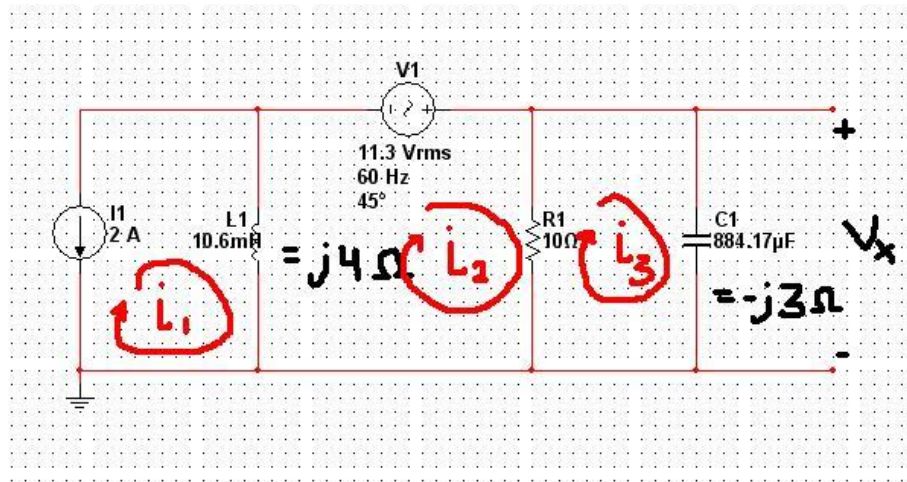

Do KVL:

$$i_1 = -2 A$$

$$j4i_2 - j4i_1 + 10i_2 - 10i_3 = 8 + j8$$

$$-j4i_1 + (10 + j4)i_2 - 10i_3 = 8 + j8$$

$$(10 + j4)i_2 - 10i_3 = 8$$

$$10i_3 - 10i_2 - j3i_3 = 0$$

$$-10i_2 + (10 - j3)i_3 = 0$$

Use Matlab to solve for i_2 and i_3 .

$$i_2 = 2.95 - j4.46 A$$

$$i_3 = 3.93 - j3.28 A$$

Now that we have i_3 , we can compute V_x using Ohm's Law.

$$V_x = i_3(-j3) = -9.83 - j11.79 V$$

Multisim Result for V_x

(Assuming a frequency of 60 Hz and omega of 377)

