

4.40 Find v_o in the circuit in Fig. P4.40.


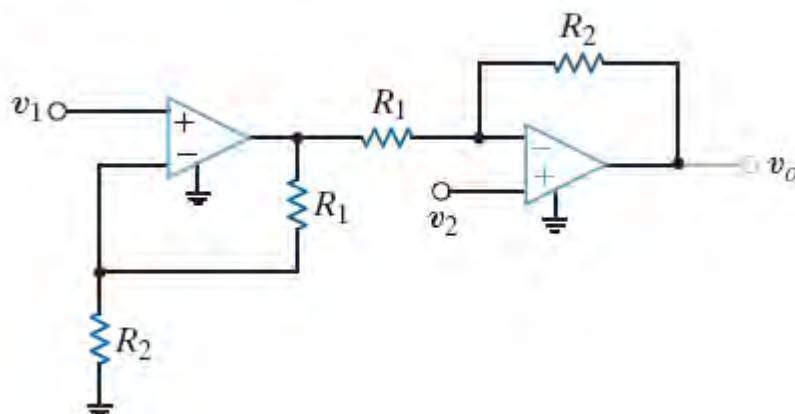


Figure P4.40

SOLUTION:

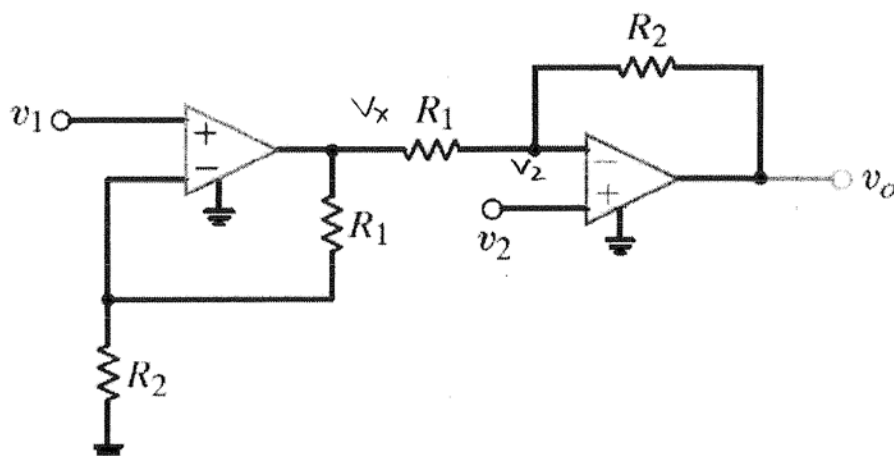

The first op-amp is a non-inverting configuration.

$$\frac{v_x}{v_1} = 1 + \frac{R_1}{R_2}$$

$$v_x = v_1 \left(\frac{R_2 + R_1}{R_2} \right)$$

KCL at v_- of the 2nd op-amp:

$$\frac{V_x - V_2}{R_1} + \frac{V_0 - V_2}{R_2} = 0$$

$$V_0 = V_2 \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_x$$

$$V_0 = V_2 \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \left(V_1 \left[\frac{R_2 + R_1}{R_2} \right] \right)$$

$$V_0 = \left(1 + \frac{R_2}{R_1} \right) (V_2 - V_1)$$

5.14 Find I_o in the circuit in Fig. P5.14 using superposition.


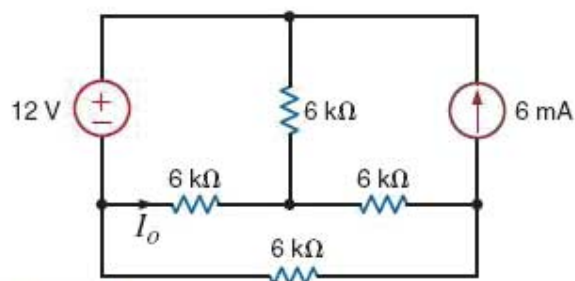



Figure P5.14


SOLUTION:

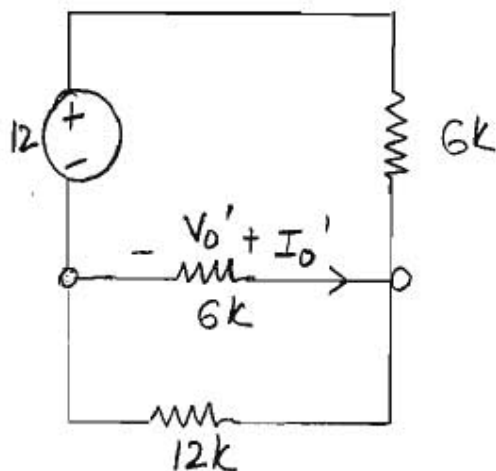

$$V_o' = (12) \left(\frac{4k}{10k} \right) = \frac{48}{10} = \frac{24}{5} \text{ V}$$
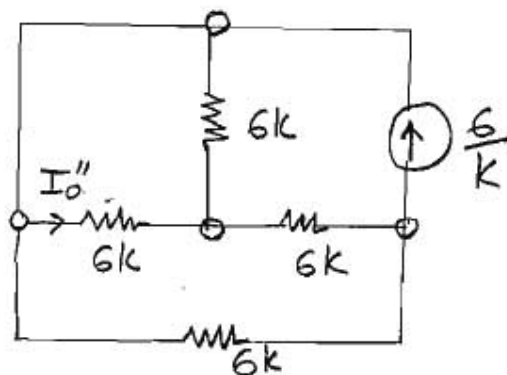
$$I_o' = \frac{-24/5}{6k} = -\frac{4}{5k} \text{ A}$$



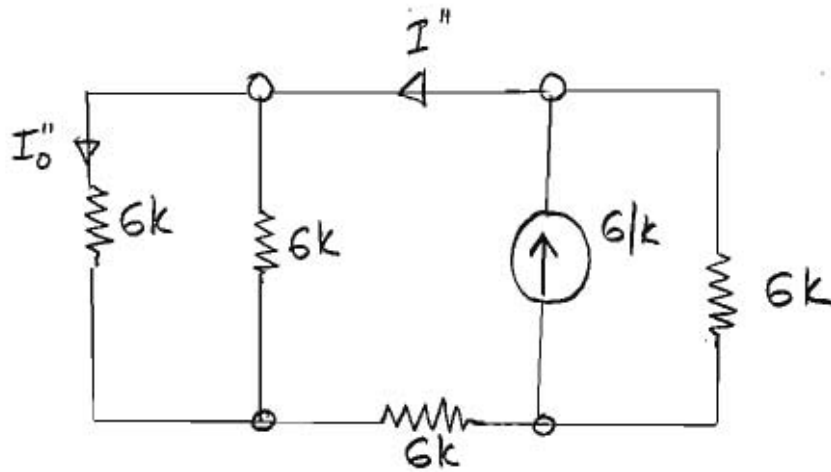

$$I'' = \frac{6}{k} \left(\frac{6k}{15k} \right) = \frac{36}{15k} = \frac{12}{5k}$$

$$I_0'' = I''/2 = \frac{6}{5k} \text{ A}$$

$$\begin{aligned} I_0 &= I_0' + I_0'' \\ &= -\frac{4}{5k} + \frac{6}{5k} \\ &= 2/5k \text{ A} \end{aligned}$$